

ECE 697CE

Foundations of Computer Engineering

Lesson 6

Verilog

Rationale


- Verilog specifies behavioral and structural definition of a digital system
- Verilog can describe exact contents of truth tables and datapath of the latest section

Objectives

- **Demonstrate familiarity with hardware design language**
- **Discuss the role of modules and its instantiation within Verilog**

Poll: Prior Knowledge

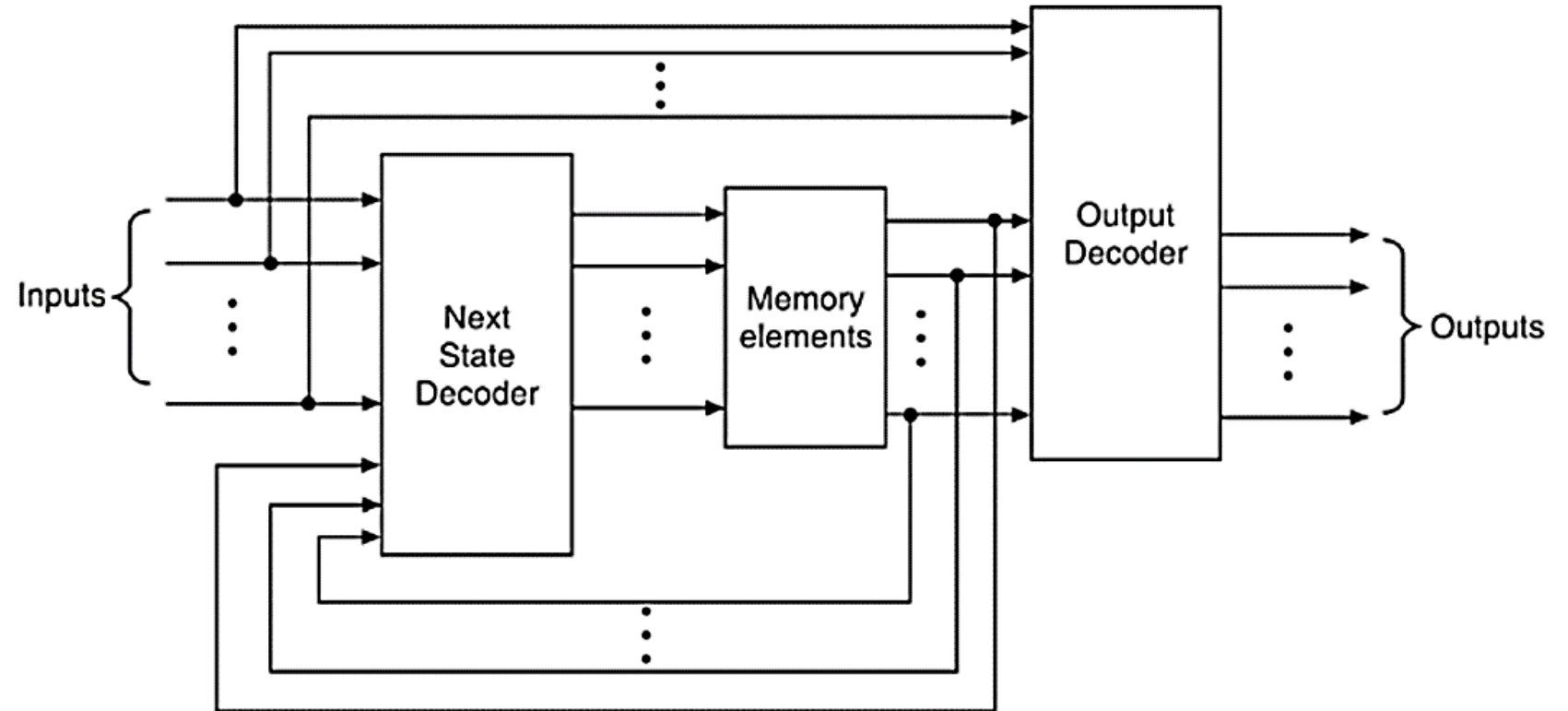The following is an example of what type of finite state machine?



- 1) Mealy Machine
- 2) Moore Machine

Prior Knowledge


- **Let's review from Lesson 4 & 5: Finite State Machines**
 - Sequential circuits
 - Mealy & Moore Machines
 - Synchronizing & Distinguishing Sequences

Orchestrated Discussion (Hand Raise): Critical Thinking Exercise

- Discuss 2 questions about Lesson 5


Introduction

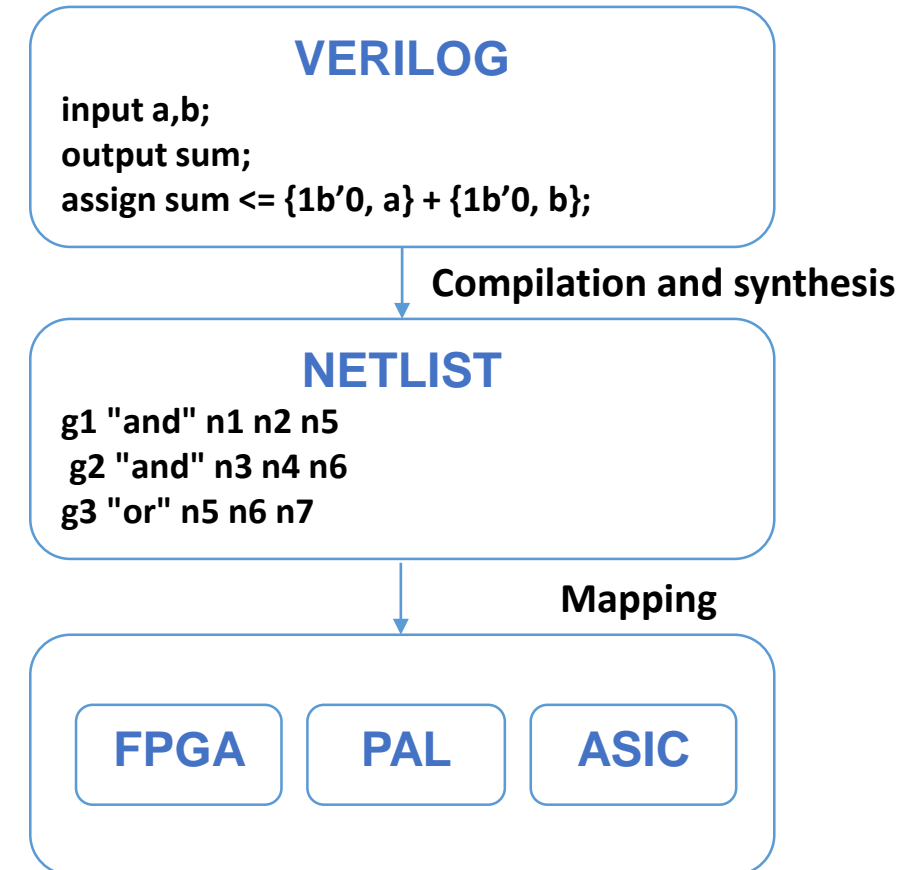- **Hardware description language: Device independent representation of digital logic**
- **Describe hardware in**
 - Behavioral level or algorithmic level
 - Data flow level
 - Gate level
 - Switch level
- HDL description compiled into a netlist
- Synthesis optimizes the logic
- Mapping targets a specific hardware platform



Typical Design Flow

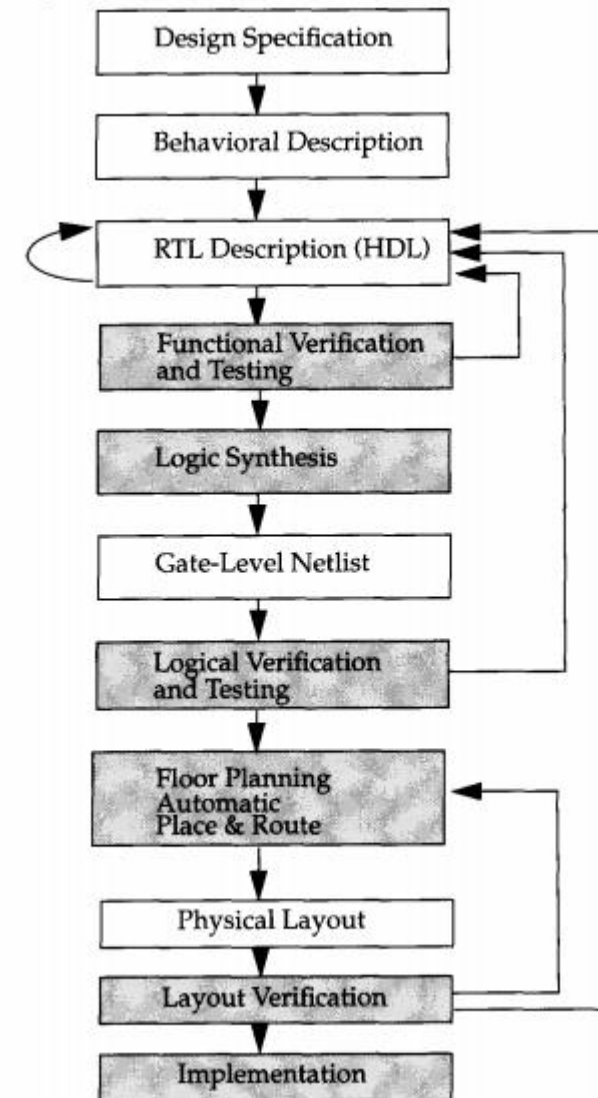Using Hardware
Description
Languages like
Verilog



Importance of HDLs


- Can write RTL description without choosing a specific fabrication technology
 - Logic synthesis tool convert the design to any fabrication technology
 - Need not redesign the circuit if a new technology emerges
- Functional verification of the design can be done at an early stage
 - Designers working at the RTL level can modify description till it meets desired functionality
 - Most design bugs can be eliminated
 - Cuts down design cycle time significantly
- Analogous to computer programming
- Concise representation of the design compared to gate level schematics

Popularity of Verilog


- Easy to learn and use
- Syntax similar to C programming language
- Allow different levels of abstraction to be mixed in the same model
- Only one language for stimulus and hierarchical design
- Most popular logic synthesis tools support Verilog HDL
- All fabrication vendors provide Verilog HDL libraries for post logic synthesis simulation.

Design Methodologies for Verilog

- Top down Design Methodology

 


- Bottom up Design Methodology

 


- Typically a combination of both is used

4 Bit Ripple Carry Counter

 


- Made of negative edge triggered Flip flops
- T Flip flops can be made from negative edge triggered D Flip flops and inverters

reset	q_n	q_{n+1}
1	1	0
1	0	0
0	0	1
0	1	0

 

Design Hierarchy for Ripple Carry Counter

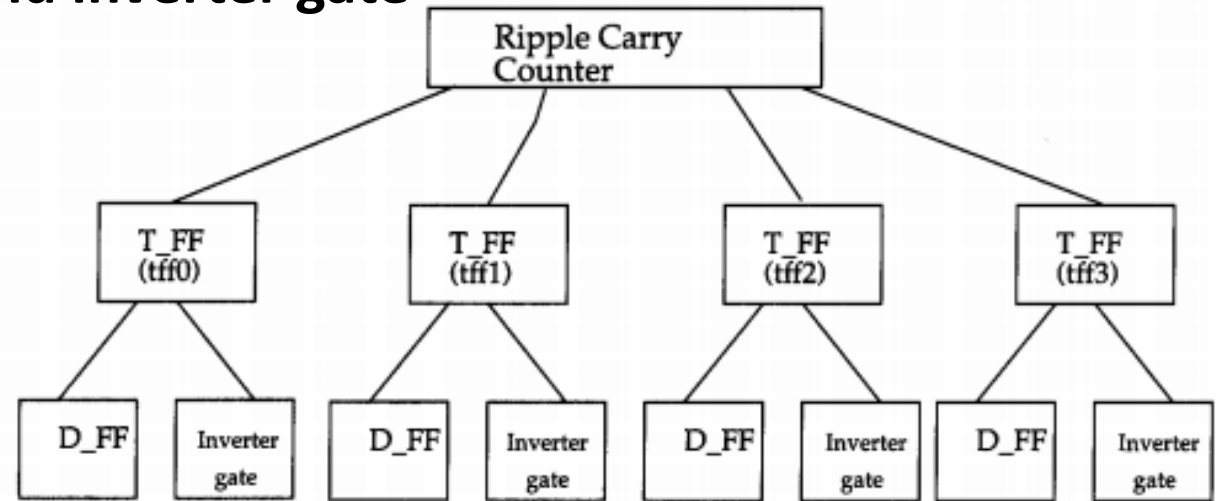
- Top down design
 - Specify functionality of Ripple carry counter (Top level block)
 - Implement counter with T flip flops
 - Build the T flip flop from D flip flop and inverter gate



- Bottom up design
 - Flows in opposite direction
 - Build D Flipflops from and, or gates
- Bottom up flow meets the top down flow at the level of D Flip flop

Orchestrated Discussion (Hand Raise): Design Hierarchy

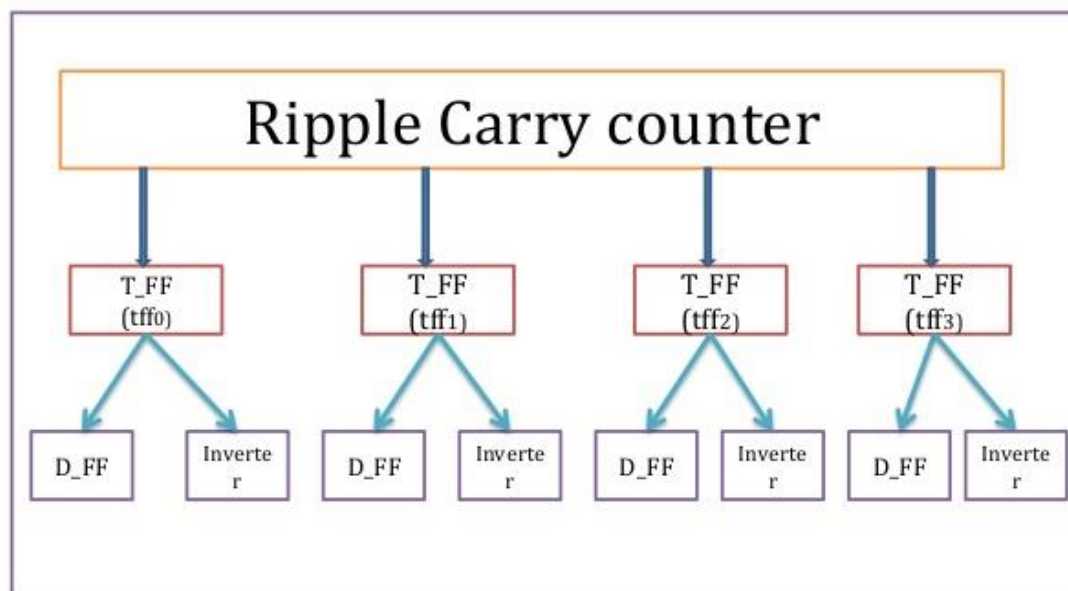- Identify whether the following example represents a top down or a bottom up design methodology



Basic Building Block in Verilog

- **Module**: Basic building block in Verilog
- Can be an element or a collection of lower level design blocks
 - Typically elements are grouped to modules and used at many places in design
- Provides necessary functionality to the higher level block using port interface
- Hides internal implementation from the higher level block
- Allows designer to modify module internals without affecting the rest of the design

```
module <module_name> (<module_terminal_list>);  
  ..  
  <module internals>  
  ..  
  ..  
endmodule
```

Modules: Ripple Carry Counter

- T_FF, D_FF are examples of modules

```
module T_FF ( q, clock, reset);  
  ..  
  <functionality of T flip flop>  
  ..  
  ..  
endmodule
```

```
module D_FF (q, d, clk, reset);  
  ..  
  <functionality of D flip flop>  
  ..  
  ..  
endmodule
```


Abstraction Levels of Verilog

- Internals of each module can be described at four levels of abstraction
- Module behavior is independent of the level of abstraction

Register Transfer level (RTL) :

- Combination of behavioral and dataflow constructs
- Code that can be synthesized i.e. acceptable to logic synthesis tools

Abstraction Levels of Verilog

Behavioral level or algorithmic level

- Highest level of abstraction
- No regard to hardware implementation details
- Design at this level : similar to C programming

Data flow level

- Specify data transfer between hardware registers
- Specify how data is processed in the design

Abstraction Levels of Verilog

Gate level


- Described by logical gates and interconnections
- Similar to design in terms of gate level logic diagram

Switch level

- Lowest level of abstraction
- Implementation in terms of switches, nodes and interconnections

Whiteboard: Abstraction Levels of Verilog

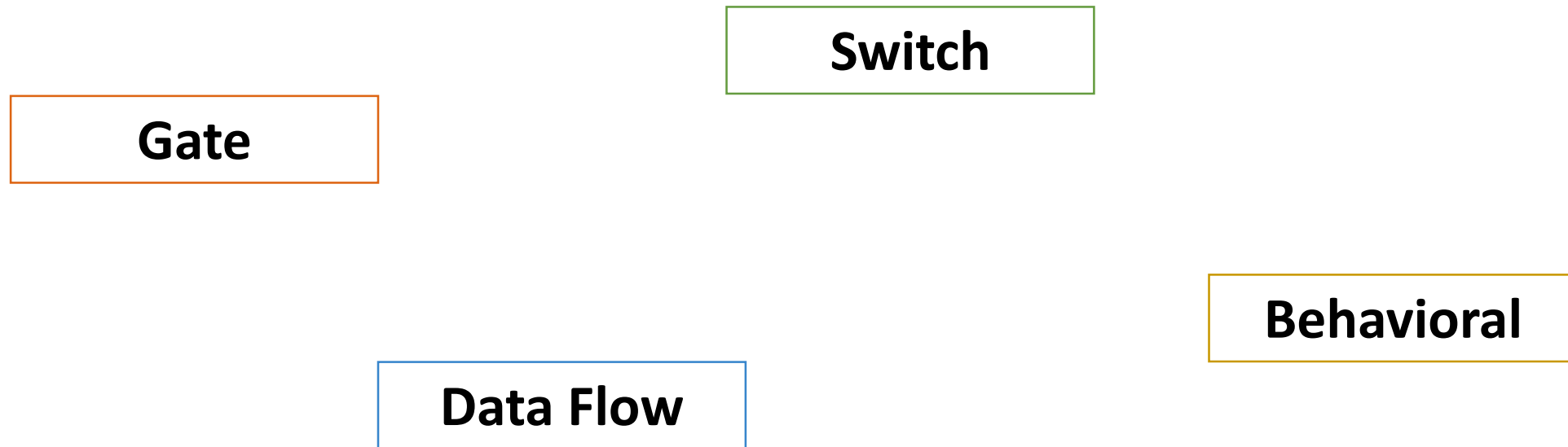Correctly organize the different levels of abstraction from highest to lowest




Instances of Modules

- Module provides templates from actual objects or instances can be created
- Process of creating objects from module template is called instantiation
- Module definition can incorporate copies of other modules by instantiating them
- Module definitions specify how the module will work
- Module must be instantiated for use in the design

Module Instances: Ripple Carry Adder
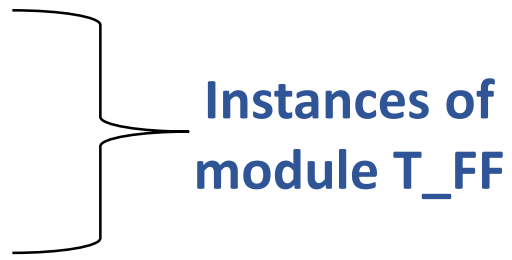
```
module ripple_carry_counter( q, clock, reset);  
output [3:0] q;  
input clk, reset;  
  
T_FF tff0(q[0], clock, reset);  
T_FF tff1(q[1], q[0], reset);  
T_FF tff2(q[2], q[1], reset);  
T_FF tff3(q[3], q[2], reset);  
endmodule
```





Instances of
module T_FF

```
module T_FF ( q, clock, reset);  
..  
<functionality of T flip flop>  
..  
..  
endmodule
```

Components of Simulation

- Functionality of the design block can be tested by applying stimulus and checking results
- Design block tested using stimulus blocks (test bench)
- 2 styles of stimulus block application
 - 1) Stimulus block becomes the top level block
 - Stimulus block instantiates the design block
 - Directly drives the signals in the design block
 - 2) Instantiate and stimulus and design block in a top level dummy module
 - Stimulus block interacts with the design block through interface

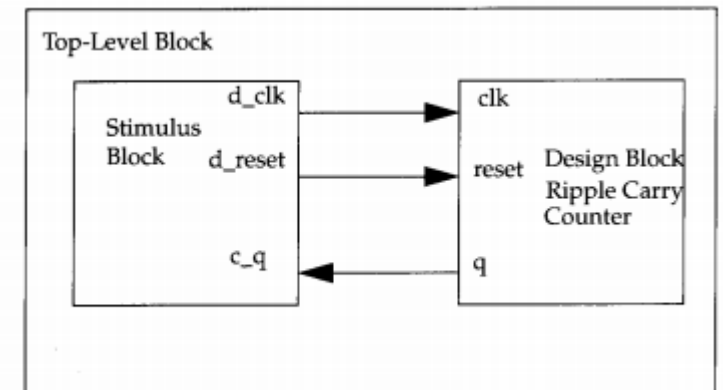 

Group Discussion and Report Back (Short Answer): Verilog Applications

- What are some potential applications of Verilog in your personal or professional experiences?

Poll: Application

In the following diagram, identify the missing component.

```
module D_FF (q, d, clk, reset);  
  ..  
  <functionality of D _____>  
  ..  
  ..  
endmodule
```

1. “reset”
2. “clock”
3. “T”
4. “flip-flop”

Summary of this Lesson

- Introduction to Verilog

To Prepare for the Next Lesson

- Read the Required Readings for Lesson 7.
- Complete the Pre-work for Lesson 7.
- Continue working on the Project.

Go to the online classroom for details.