

ECE 697CE

Foundations of Computer Engineering

Lesson 4 & 5

Finite State Machines

Rationale


- Sequential circuits have states that store the effect of previously applied inputs
- Number of states for practical implementations is finite or limited
- Moore Machine: output associated to current state only
 - state \rightarrow output
- Mealy Machine: output associated to both state and specific input
 - (state, input) \rightarrow output

Objectives

- **Apply the principles of finite state machine to create sequential circuits.**
- **Sequential circuits have outputs that are based on its inputs and current state.**

Poll: Prior Knowledge

 The provided figure is an example of what?



- 1) Monotonic Function
- 2) Minimization
- 3) Fault Detection
- 4) Don't Care Combination
- 5) Karnaugh Map

Prior Knowledge

- **State-less circuit = current inputs alone determine the output**
- **Let's review from Lesson 2: Boolean Switching Functions**
 - **Minimization**
 - **Karnaugh Map**
 - **Unate & Monotonic Functions**
 - **Symmetric Functions**

Orchestrated Discussion (Hand Raise): Critical Thinking Exercise

- Discuss two questions about the previous lesson.

Digital Circuits Classification and Basic building Blocks

- **Combinational circuits**: Output = Function of (external inputs)
- **Sequential circuit**: Output = Function of (external inputs + stored information)
- **Synchronous Vs. Asynchronous Sequential Circuits**
- **Flip-Flops the building blocks of Sequential Circuits**
 - Latches Vs Flip-Flops
 - Flip-Flop types:
 - JK-Type
 - D-Type
 - T-Type

Sequential Circuits and Finite State Machines

- **Sequential circuit**: Output = Function of (external inputs + stored information)
- **Finite-state machine (FSM)**: abstract model to describe the synchronous sequential machine and its spatial counterpart, the iterative network
- **Example**: Serial binary adder: block diagram, addition process, state table and state diagram

 


Fig: Block diagram

$$\begin{array}{rcccccc}
 & t_5 & t_4 & t_3 & t_2 & t_1 & \\
 & 0 & 1 & 1 & 0 & 0 & = X_1 \\
 + & 0 & 1 & 1 & 1 & 0 & = X_2 \\
 \hline
 & 1 & 1 & 0 & 1 & 0 & = Z
 \end{array}$$

Fig: Addition process

Internal States of Machines

Serial adder:

- Output at time t_i is a function of
 - Input values at the time x_1 and x_2
 - Carry generated at t_{i-1}
- Carry in turn depends on input at t_{i-1} and carry at t_{i-2} and so on
- State A means no carry was produced, state B means a carry was produced in the previous add.
- Use internal states to preserve information regarding input values from the time it is set to operating
- State diagram and state tables describe the behavior

<i>PS</i>	<i>NS, z</i>			
	$x_1x_2 = 00$	01	11	10
A	A, 0	A, 1	B, 0	A, 1
B	A, 1	B, 0	B, 1	B, 0

Fig: State table

 


Fig: State diagram

Finite State Machines

Finite State Machines: Machines whose past histories can affect their future behavior in only finite number of ways.

- **Serial adder:**
 - Response to signal at time t is only a function of input at t and carry at $t - 1$
 - Group input histories to 2 classes:
 - Those resulting in a 1 carry at t
 - Those resulting in a 0 carry at t
- Every FSM contains a finite number of latches used to encode the current state.
- The current state stores information about the previous inputs.

Finite-State Model

Deterministic machines:

- Next state $S(t + 1)$ determined uniquely by
 - present state $S(t)$
 - present input $x(t)$

- State transition function $\rightarrow \delta$


$$S(t + 1) = \delta \{S(t), x(t)\}$$

- Output function $\rightarrow \lambda$

Mealy machine : $z(t) = \lambda \{S(t), x(t)\}$

Moore machine : $z(t) = \lambda \{S(t)\}$

Video: Finite-State Model

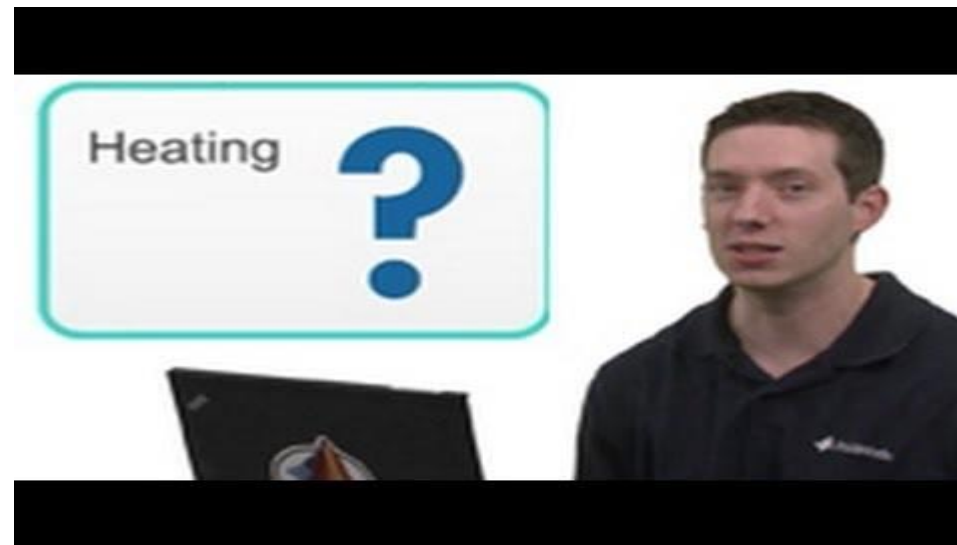

A Typical Mealy Model

- Mealy machine: Output depends on the present state and the present inputs
- A Mealy model:
 - 2 D flip flops
 - Input $x(t)$
 - Output $z(t)$

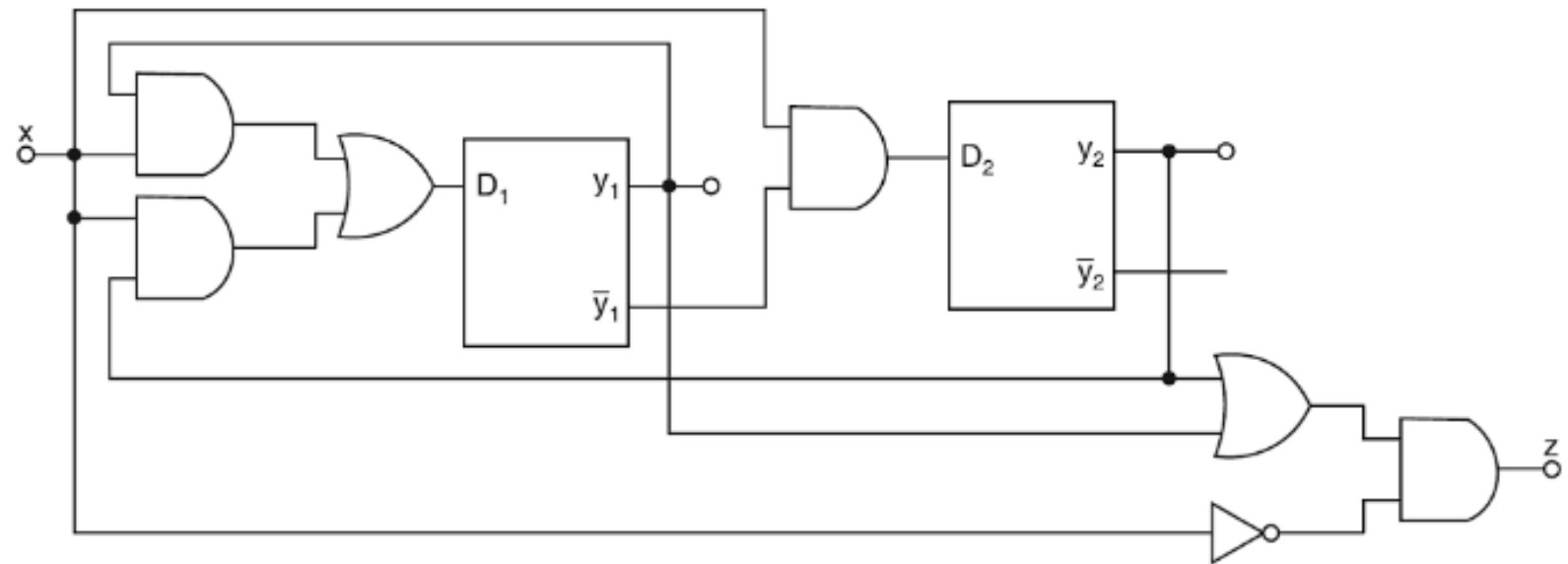


Fig: Logic diagram of a typical Mealy circuit

A Typical Mealy Model

- D input of flip-flop determines the next state value
- Typical state equations
 - $y_1(t + 1) = y_1(t)x(t) + y_2(t)x(t)$
 - $y_2(t + 1) = \bar{y}_1(t)x(t)$
- Typical output equation
 - $z(t) = \{y_1(t) + y_2(t)\} \bar{x}(t)$

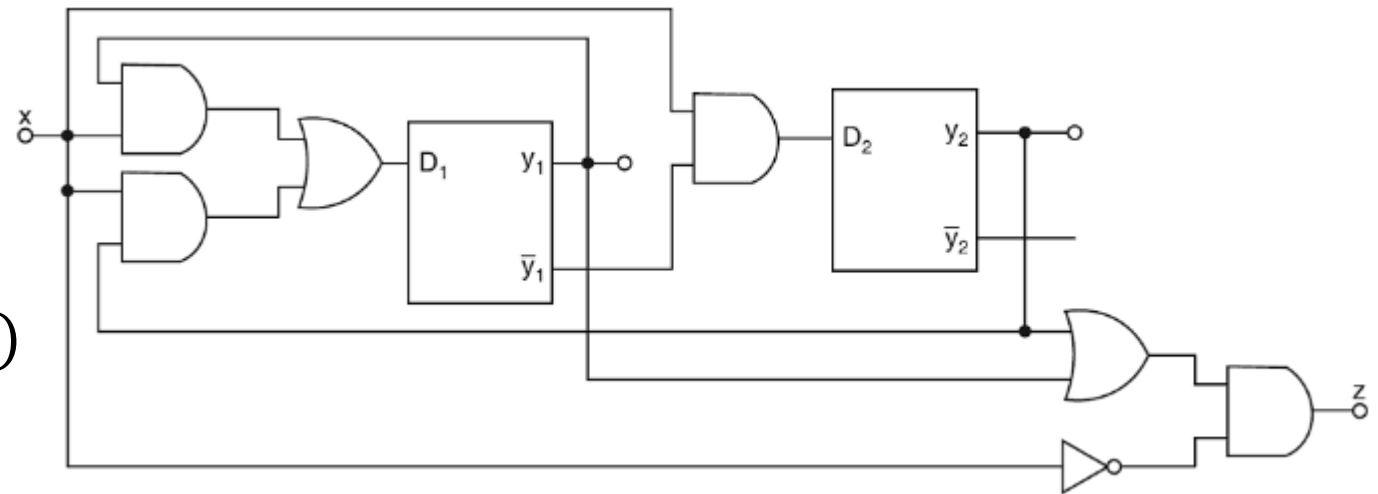


Fig: Logic diagram of a typical Mealy circuit

A Typical Mealy Model

PS		NS				O/P	
		x = 0		x = 1		x = 0	x = 1
y ₁	y ₂	Y ₁	Y ₂	Y ₁	Y ₂	z	z
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

Fig: State table

 


Fig: State diagram

Mealy Circuit Model

- Block schematic of a Mealy Circuit Model

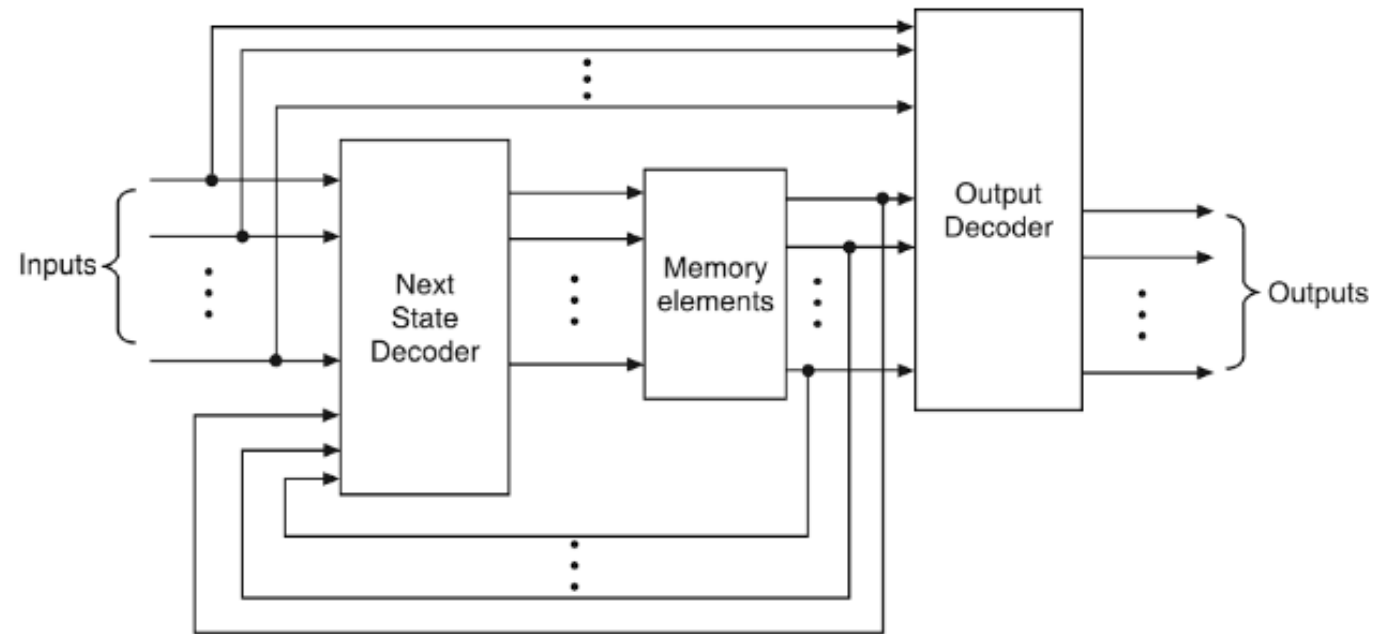


Fig: Mealy circuit model

A Typical Moore Model

- Moore Machine: Output depends only on the present state of the system
- A typical Moore model:
 - 2 T flip-flops
 - Input $x(t)$
 - Output $z(t)$

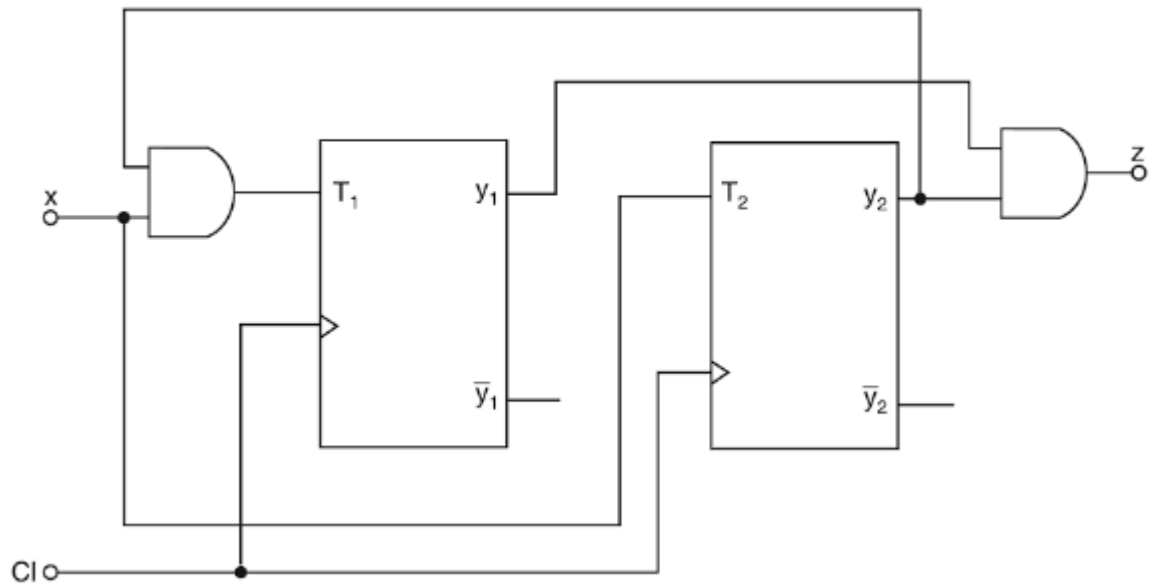


Fig: Logic diagram of a Moore model

A Typical Moore Model

- Input $x(t)$ is used only to determine the inputs of flip-flops
- Its state equations
 - $y_1(t + 1) = y_2(t)x(t) \oplus y_1(t)$
 - $y_2(t + 1) = x(t) \oplus y_2(t)$
- Its output equations
 - $z(t) = y_1(t)y_2(t)$

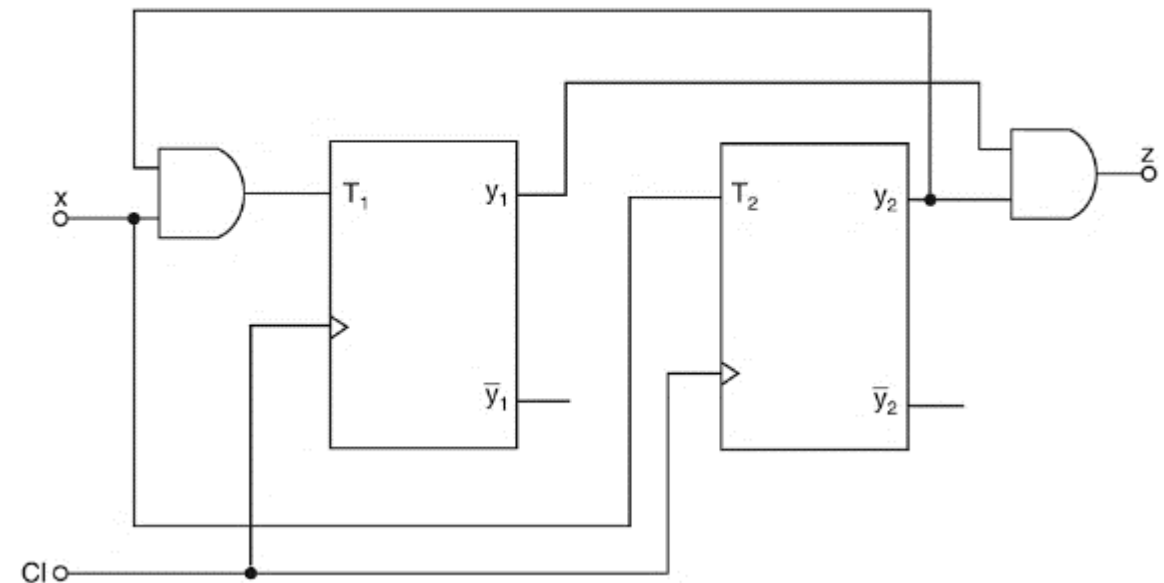


Fig: Logic diagram of a Moore model

A Typical Moore Model

PS		NS				O/P
		x = 0		x = 1		
y ₁	y ₂	Y ₁	Y ₂	Y ₁	Y ₂	z
0	0	0	0	0	1	0
0	1	0	1	1	0	0
1	0	1	0	1	1	0
1	1	1	1	0	0	1

Fig: State table

 


Fig: State diagram

Moore Circuit Model

- Block schematic of a Moore Model

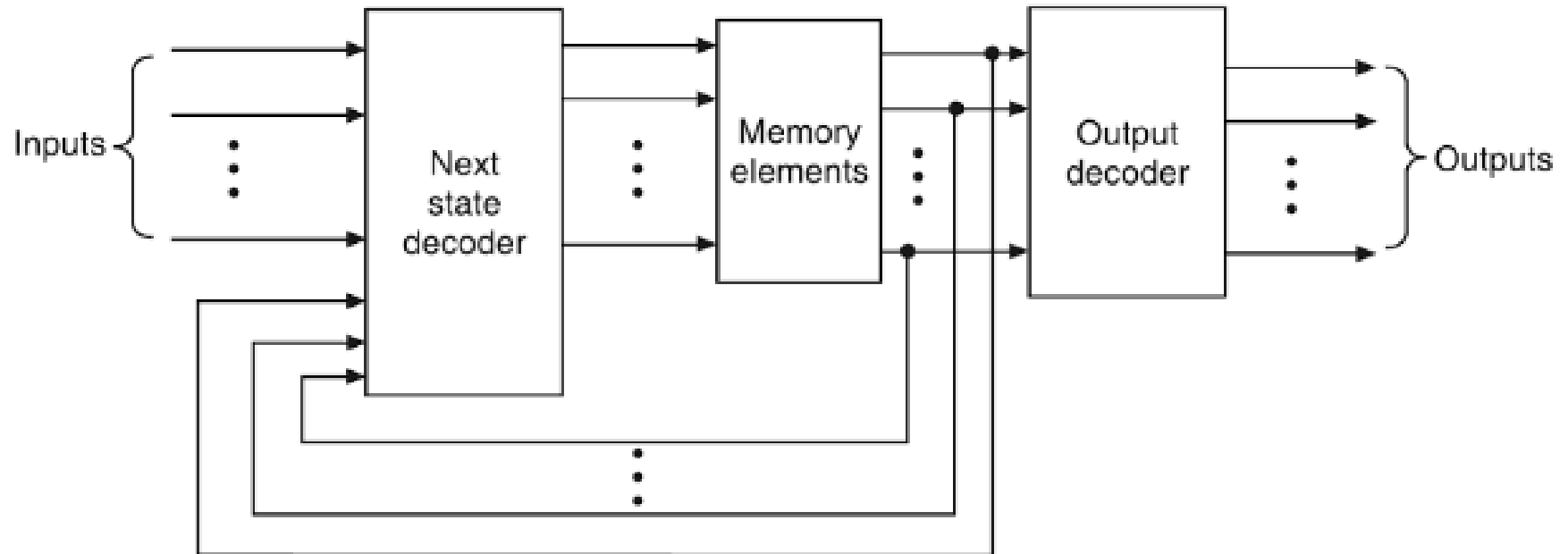


Fig: Moore circuit model

Group Discussion and Report Back (Pen): Mealy and Moore Models

- Using the provided circuit models, identify at least 3 differences between the Mealy and Moore models.

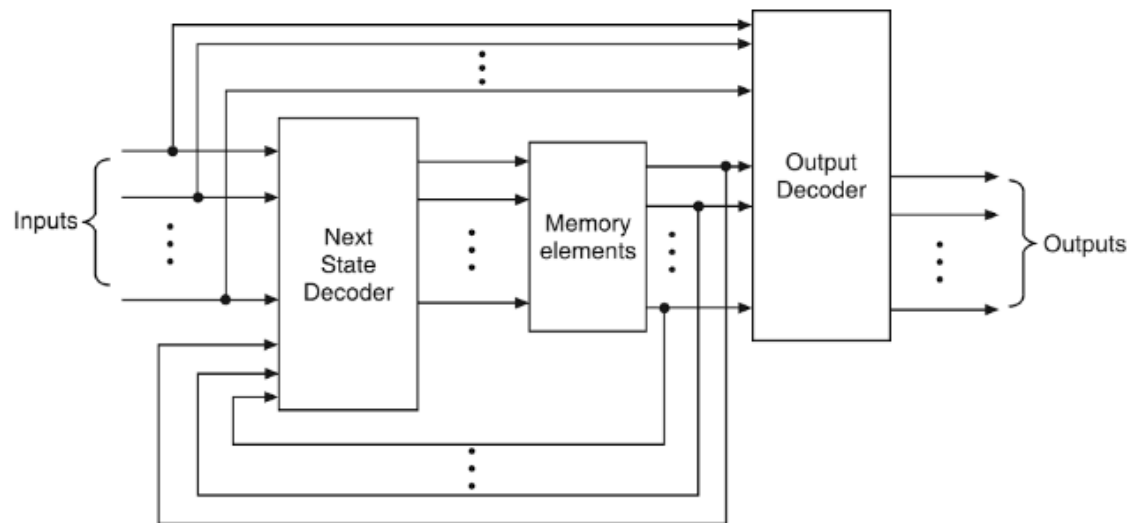


Fig 1: Mealy circuit model

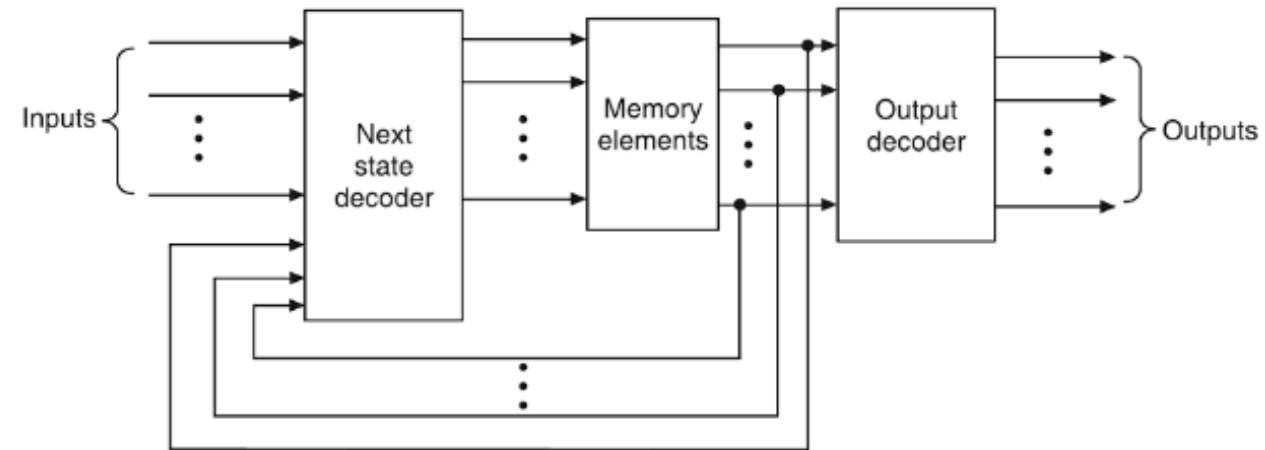


Fig 2: Moore circuit model

Sequence Detector for Moore Model

- Sequence detector for 01 or 10.
- Output 1 when the sequence is seen
- Moore Model: Output is a function of only state

 


Fig: State diagram

reset	input	current state	next state	output
1	—	—	A	
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	D	0
0	0	C	E	0
0	1	C	C	0
0	0	D	E	1
0	1	D	C	1
0	0	E	B	1
0	1	E	D	1

Fig: State table

Sequence Detector for Mealy Model

- Sequence detector for 01 or 10
- Output 1 when the sequence is seen
- Mealy Model: Output is a function of state and inputs

 


Fig: State diagram

reset	input	current state	next state	output
1	–	–	A	0
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	C	1
0	0	C	B	1
0	1	C	C	0

Fig: State table

Homing Sequence

Homing sequence is $X=101$, since the final state can be uniquely determined by observing outputs.

Starting at A, we end-up in state C with outputs 100

Starting at B, we end-up in state A with outputs 100

Starting at C, we end-up in state B with outputs 101


Starting at D, we end-up in state C with outputs 011

Present State	Input $X=0$	Input $X=1$
A	C,1	D,0
B	D,0	B,1
C	B,0	C,1
D	C,0	A,0

If we observe outputs, at the end of 3rd input, we know the current state, even though the initial state was unknown

Distinguishing Sequence

- A sequence X is a distinguishing sequence for machine M if the output sequence produced in response to X is distinct for each initial state.
- Distinguishing = separating for nondeterministic machines
- A distinguishing (input) sequence α allows to determine the initial state of the machine under experiment
- After applying α at any state s and observing an output response β the initial state s becomes known

 

$$out(s_i, \alpha) \cap out(s_j, \alpha) = \emptyset$$

Fig: Distinguishing sequence α

Synchronizing Sequence

- A synchronizing sequence is a sequence of inputs that will force the machine to a specified final state independent of the initial state or output sequence.
- A synchronizing sequence α takes the machine under experiment to a given state after applying α
- After applying α at any state the final state is s'

 


Fig: Synchronizing sequence α

Summary of this Lesson

- Introduction to Finite State Machines (FSMs)
- Moore FSM Machines
- Mealy FSM Machines
- Sequence Detector Machines
- Introduction to Special Sequences

Post-work for Lesson 5

Homework

- After the Live Lecture, you will complete and submit a homework assignment. Go to the online classroom to view and submit the assignment.

To Prepare for the Next Lesson

- Read the Required Readings for Lesson 6.
- Complete the Pre-work for Lesson 6.
- Start working on the Project 1.

Go to the online classroom for details.