

ECE 697CE

Foundations of Computer Engineering

Lesson 3

Boolean Switching Functions (Continued)

Rationale

- Minimizing switching functions helps overcome limitations of switching algebra
- Minimization also creates more effective expressions

Objectives

- Apply principles of minimization to simplify switching functions
- Compare the properties of unate, monotonic, and symmetric functions

Poll: Prior Knowledge

The following is an example of what principle of Boolean Switching Functions?

$$[[f(x_1, x_2 \dots x_n, 0, 1, +, \cdot)]']' = f(x_1, x_2 \dots x_n, 0, 1, +, \cdot)$$

1. Combinational Switching Logic
2. De Morgan's Theorem
3. Law of Complementation
4. Consensus Theorem

Prior Knowledge

- **Let's review from Lesson 1: Boolean Switching Functions**
 - Number representation
 - Switching logic & algebra
 - Simplification of expressions
 - De Morgan's Theorems
 - Threshold logic

Orchestrated Discussion (Hand Raise): Critical Thinking Exercise

- Discuss two questions regarding Lesson 2.

Minimization Example

- Example: $f(w, x, y, z) = \sum(1, 5, 6, 7, 11, 12, 13, 15)$

- One irredundant form:

$$f = wxy' + wyz + w'xy + w'y'z$$

- Dotted box: xz is redundant

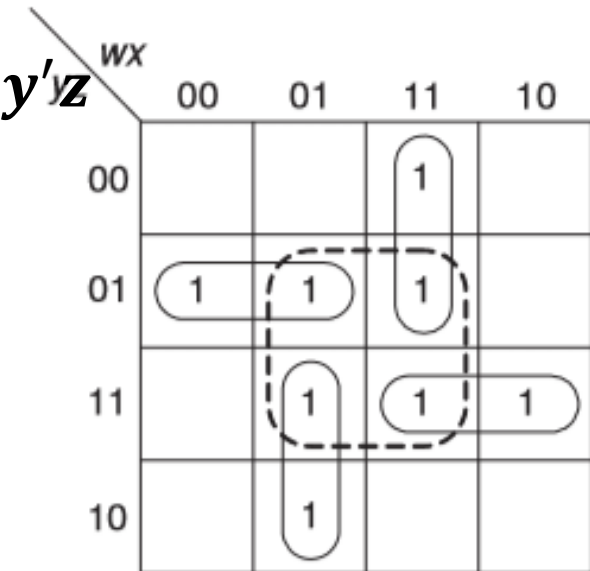


Fig : Map for $f = wxy' + wyz + w'xy + w'y'z$

Group Discussion and Report Back (Pen): Minimization

- Minimize the following problem using the Karnaugh maps method.

$$Z = f(A,B,C) = \bar{A}\bar{B}\bar{C} + \bar{A}B + AB\bar{C} + AC$$

Minimization

- Minimize the following problem using the Karnaugh maps method.

$$Z = f(A,B,C) = \bar{A}\bar{B}\bar{C} + \bar{A}B + AB\bar{C} + AC$$

AB \ C		00	01	11	10
C	0	1	1	1	
	1		1	1	1

Don't Care Combinations

- Don't care combination \emptyset
 - Combination for which the value of the function is not specified
 - Either input combinations may be invalid
 - Or precise output value is of no importance
- A function with k don't cares corresponds to a class of 2^k distinct functions
- Choose the function with the minimal representation
 - Assign 1 to some don't cares and 0 to others in order to increase the size of the selected cubes
 - No cube containing only don't care cells may be formed

Code Converter for Don't Care Combinations

- Example: Code converter from BCD to excess-3
- Combinations 10 through 15 are don't cares

Decimal number	BCD inputs				Excess-3 outputs			
	w	x	y	z	f ₄	f ₃	f ₂	f ₁
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

Fig : Truth table for code converter

- Output functions

$$f_1 = \sum (0, 2, 4, 6, 8) + \sum_{\emptyset} (10, 11, 12, 13, 14, 15) \quad f_3 = \sum (1, 2, 3, 4, 9) + \sum_{\emptyset} (10, 11, 12, 13, 14, 15)$$

$$f_2 = \sum (0, 3, 4, 7, 8) + \sum_{\emptyset} (10, 11, 12, 13, 14, 15) \quad f_4 = \sum (5, 6, 7, 8, 9) + \sum_{\emptyset} (10, 11, 12, 13, 14, 15)$$

Code Converter for Don't Care Combinations

- Minimal functions from Maps

$$\begin{aligned}
 f_1 &= z' \\
 f_2 &= y'z' + yz \\
 f_3 &= x'y + x'z + xy'z' \\
 f_4 &= w + xy + xz
 \end{aligned}$$

yz \ wx	00	01	11	10
00	1	1	ϕ	1
01			ϕ	
11			ϕ	ϕ
10	1	1	ϕ	ϕ

 f_1 map

yz \ wx	00	01	11	10
00	1	1	ϕ	1
01			ϕ	
11	1	1	ϕ	ϕ
10			ϕ	ϕ

 f_2 map

yz \ wx	00	01	11	10
00		1	ϕ	
01	1		ϕ	1
11	1		ϕ	ϕ
10	1		ϕ	ϕ


 f_3 map

yz \ wx	00	01	11	10
00			ϕ	1
01		1	ϕ	1
11		1	ϕ	ϕ
10		1	ϕ	ϕ

 f_4 map

Logical Network for Code Converter

- Two-level AND-OR realization

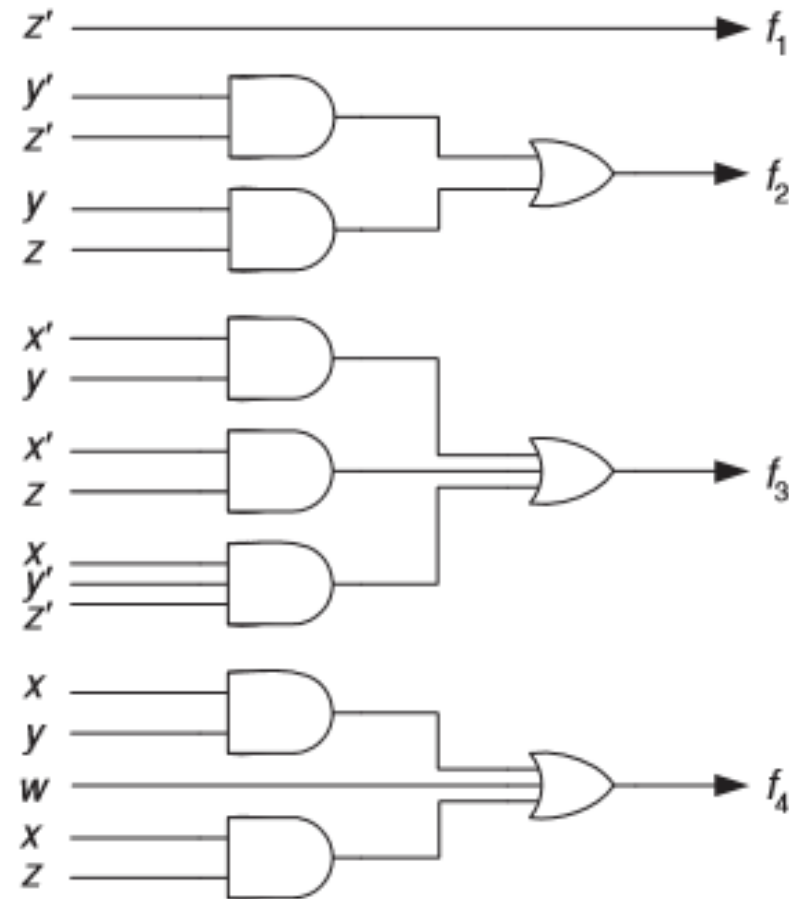

Unate Functions

Consider a function $f(x_1, x_2, \dots, x_n)$

If f is either positive or negative in x_j , it is said to be UNATE in x_j

- Examples:

1. $f(x_1, x_2, \dots, x_n) = x_1'x_2 + x_2'x_3$

- Function f is
 - Unate and negative in x_1
 - Unate and positive in x_3
 - Not Unate in x_2

Unate Functions

Consider a function $f(x_1, x_2, \dots, x_n)$
If f is unate in each of its variables, f is said to be UNATE

- **Examples:**

1. $f(x_1, x_2, \dots, x_n) = x_1'x_2 + x_1x_2x_3'$

- Function f is Unate as it can be simplified to

$$f(x_1, x_2, \dots, x_n) = x_1'x_2 + x_2x_3'$$


- Positive Unate in x_2 , negative Unate in x_1 and x_3

2. $f(x_1, x_2, \dots, x_n) = x_1x_2' + x_1'x_2$

- Function f is not Unate in either variable

Fault Detection in Functions

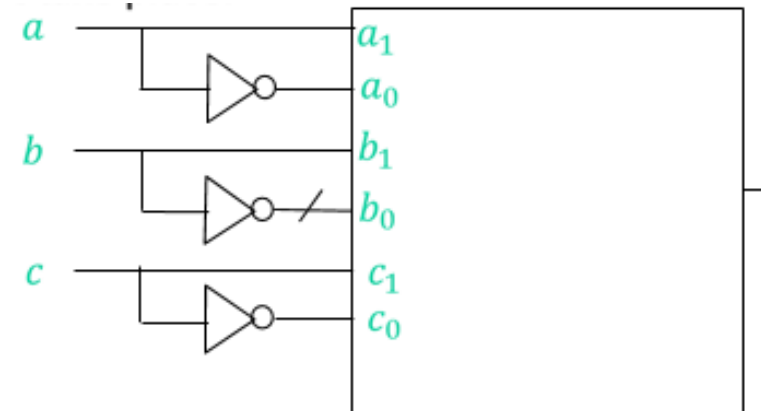- Let $f = ab'c + a'b'c + abc'$: Binate function
- Make it Unate by the following substitutions
 - $a_0 = a', a_1 = a$
 - $b_0 = b', b_1 = b$
 - $b_0 = c', c_1 = c$
- $F = a_1b_0c_1 + a_0b_0c_1 + a_1b_1c_0$: Unate function
- Unidirectional change in output



$f = 0$ for $(a, b, c) = (0, 1, 1)$

$f = 1$ for $(a, b, c) = (0, 1, 1)$ and $b_0 = 1$

Symmetric Functions

- A function of n variables x_1, x_2, \dots, x_n is symmetric if and only if the interchange of any pair of variables leaves the function identically the same
- Examples:
 - $xy' + x'y$ is symmetric in x and y
 - $xyz + x'y'z'$ is symmetric in x, y and z
- If a function is symmetric, then the number of variables taking the value 1 determines the function rather than the specific assignment of 1's among the variables

Poll: Function Classification

Classify the following function:

$$k(A, B, C) = A'B + A'C$$

1. Unate
2. Binate
3. Symmetric

Summary of this Lesson

- Minimization of Boolean functions
- Don't care conditions
- Special functions (Unate, Symmetric)

Post-work for Lesson 3

Homework

- After the Live Lecture, you will complete and submit a homework assignment. Go to the online classroom to view and submit the assignment.

To Prepare for the Next Lesson

- Read the Required Readings for Lesson 4.
- Complete the Pre-work for Lesson 4.
- Start working on the Project.

Go to the online classroom for details.