

# ECE 697CE

# Foundations of Computer Engineering

## Lesson 5

## Finite State Machines

# Rationale


- Sequential circuits have states that store the effect of previously applied inputs
- Number of states for practical implementations is finite or limited
- Moore Machine: output associated to current state only
  - state  $\rightarrow$  output
- Mealy Machine: output associated to both state and specific input
  - (state, input)  $\rightarrow$  output

# Objectives

- **Apply the principles of finite state machine to create sequential circuits.**
- **Sequential circuits have outputs that are based on its inputs and current state.**
 
# Poll: Prior Knowledge

The provided figure is an example of what?



- 1) Monotonic Function
- 2) Minimization
- 3) Fault Detection
- 4) Don't Care Combination
- 5) Karnaugh Map

# Prior Knowledge

- **State-less circuit = current inputs alone determine the output**
- **Let's review from Lesson 2: Boolean Switching Functions**
  - **Minimization**
  - **Karnaugh Map**
  - **Unate & Monotonic Functions**
  - **Symmetric Functions**

# Orchestrated Discussion (Hand Raise): Critical Thinking Exercise

- Discuss two questions about the previous lesson.

# Sequential Circuits and Finite State Machines

- **Sequential circuit**: Output = Function of ( external inputs + stored information)
- **Finite-state machine (FSM)**: abstract model to describe the synchronous sequential machine and its spatial counterpart, the iterative network
- **Example**: Serial binary adder: block diagram, addition process, state table and state diagram

 


Fig: Block diagram

$$\begin{array}{rccccc}
 & t_5 & t_4 & t_3 & t_2 & t_1 \\
 & 0 & 1 & 1 & 0 & 0 = X_1 \\
 + & 0 & 1 & 1 & 1 & 0 = X_2 \\
 \hline
 & 1 & 1 & 0 & 1 & 0 = Z
 \end{array}$$

Fig: Addition process

# Internal States of Machines

## Serial adder:

- Output at time  $t_i$  is a function of
  - Input values at the time  $x_1$  and  $x_2$
  - Carry generated at  $t_{i-1}$
- Carry in turn depends on input at  $t_{i-1}$  and carry at  $t_{i-2}$  and so on
- State A means no carry was produced, state B means a carry was produced in the previous add.
- Use internal states to preserve information regarding input values from the time it is set to operating
- State diagram and state tables describe the behavior

	$NS, z$			
$PS$	$x_1x_2 = 00$	01	11	10
A	A, 0	A, 1	B, 0	A, 1
B	A, 1	B, 0	B, 1	B, 0

Fig: State table

 


Fig: State diagram



# Finite State Machines

**Finite State Machines:** Machines whose past histories can affect their future behavior in only finite number of ways.

- 
- Serial adder:
  - Response to signal at time  $t$  is only a function of input at  $t$  and carry at  $t - 1$
  - Group input histories to 2 classes:
    - Those resulting in a 1 carry at  $t$
    - Those resulting in a 0 carry at  $t$
- Every FSM contains a finite number of latches used to encode the current state.
- The current state stores information about the previous inputs.

# Finite-State Model

## Deterministic machines:

- Next state  $S(t + 1)$  determined uniquely by
  - present state  $S(t)$
  - present input  $x(t)$

- State transition function  $\rightarrow \delta$


$$S(t + 1) = \delta \{S(t), x(t)\}$$

- Output function  $\rightarrow \lambda$

Mealy machine :  $z(t) = \lambda \{S(t), x(t)\}$

Moore machine :  $z(t) = \lambda \{S(t)\}$

# Video: Finite-State Model

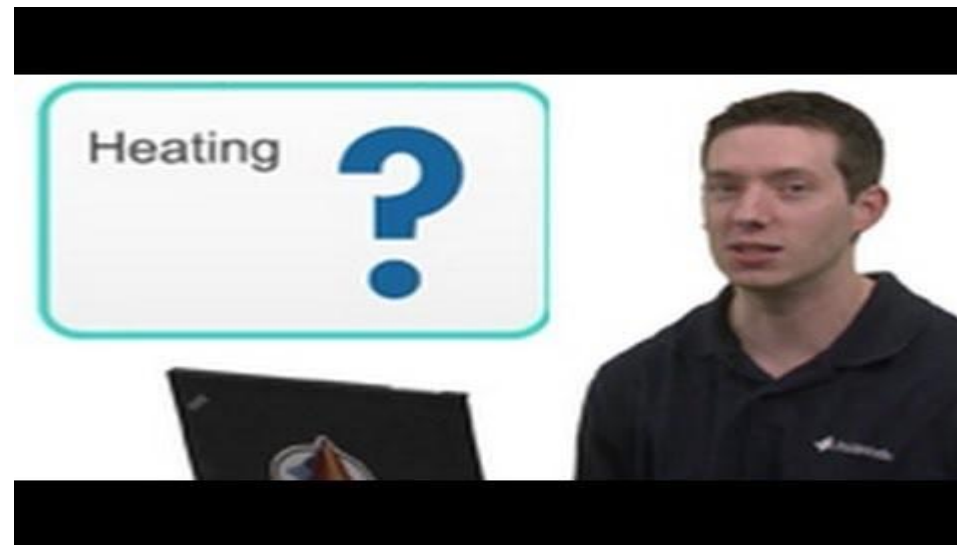

# A Typical Mealy Model

- Mealy machine: Output depends on the present state and the present inputs
- A Mealy model:
  - 2 D flip flops
  - Input  $x(t)$
  - Output  $z(t)$


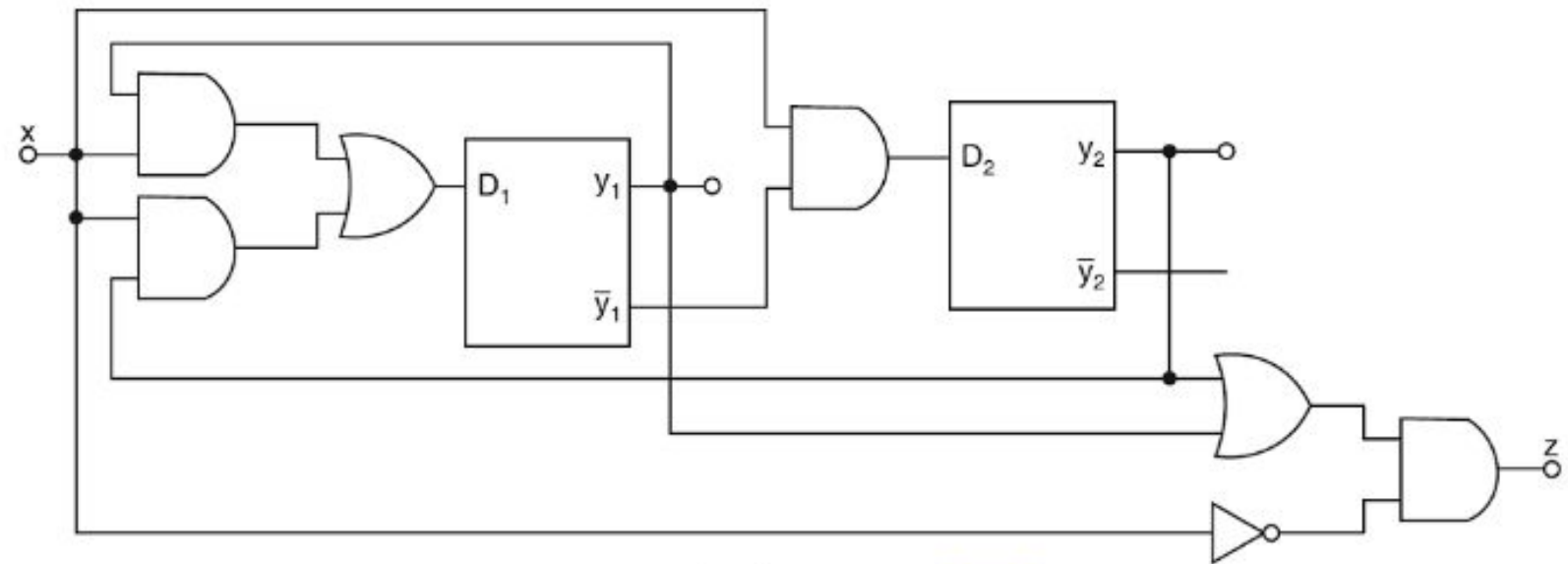


Fig: Logic diagram of a typical Mealy circuit

# A Typical Mealy Model

- D input of flip-flop determines the next state value
  - Typical state equations
    - $y_1(t + 1) = y_1(t)x(t) + y_2(t)x(t)$
    - $y_2(t + 1) = \overline{y_1}(t)x(t)$
  - Typical output equation
    - $z(t) = \{y_1(t) + y_2(t)\} \bar{x}(t)$
- 

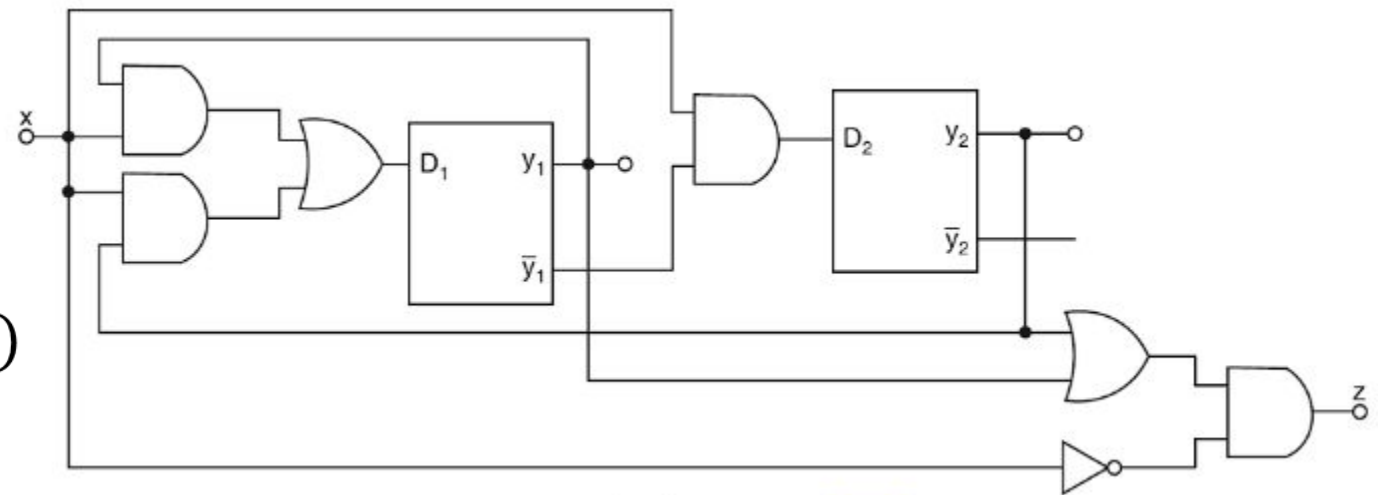

**Fig: Logic diagram of a typical Mealy circuit**

# A Typical Mealy Model

PS		NS				O/P	
		x = 0		x = 1		x = 0	x = 1
y <sub>1</sub>	y <sub>2</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>2</sub>	z	z
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

Fig: State table

 


Fig: State diagram

# Mealy Circuit Model

- Block schematic of a Mealy Circuit Model

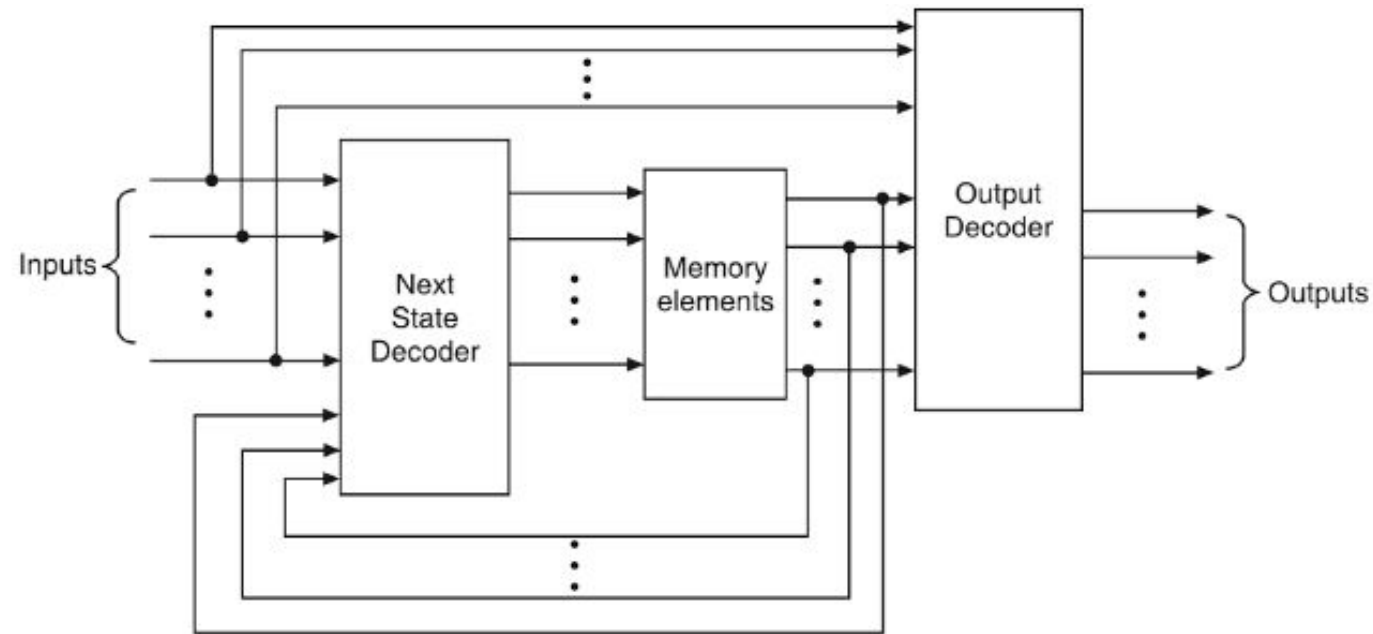


Fig: Mealy circuit model

# A Typical Moore Model

- Moore Machine: Output depends only on the present state of the system
- A typical Moore model:
  - 2 T flip-flops
  - Input  $x(t)$
  - Output  $z(t)$

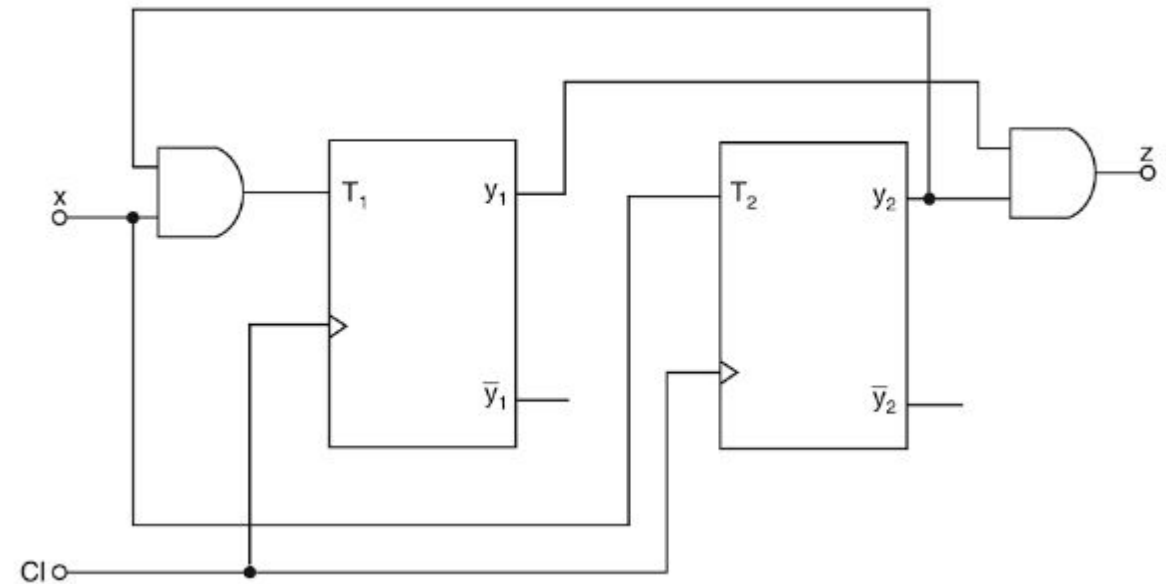


Fig: Logic diagram of a Moore model



# A Typical Moore Model

- Input  $x(t)$  is used only to determine the inputs of flip-flops
- Its state equations
  - $y_1(t+1) = y_2(t)x(t) \oplus y_1(t)$
  - $y_2(t+1) = x(t) \oplus y_2(t)$
- Its output equations
  - $z(t) = y_1(t)y_2(t)$

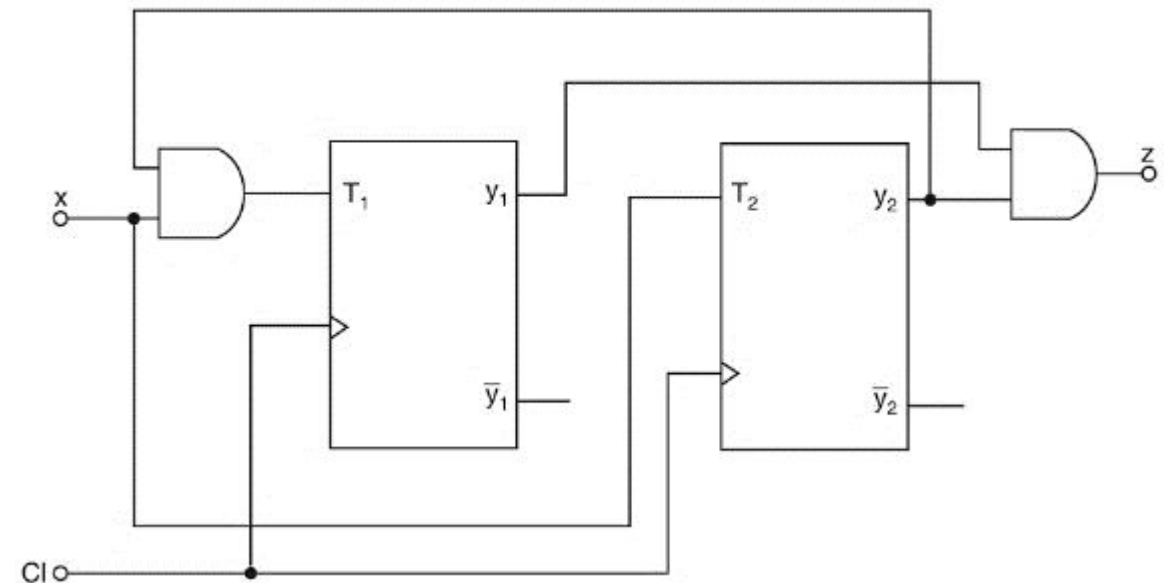


Fig: Logic diagram of a Moore model

# A Typical Moore Model

PS		NS				O/P
		x = 0		x = 1		
y <sub>1</sub>	y <sub>2</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>2</sub>	z
0	0	0	0	0	1	0
0	1	0	1	1	0	0
1	0	1	0	1	1	0
1	1	1	1	0	0	1

Fig: State table

 


Fig: State diagram

# Moore Circuit Model

- Block schematic of a Moore Model

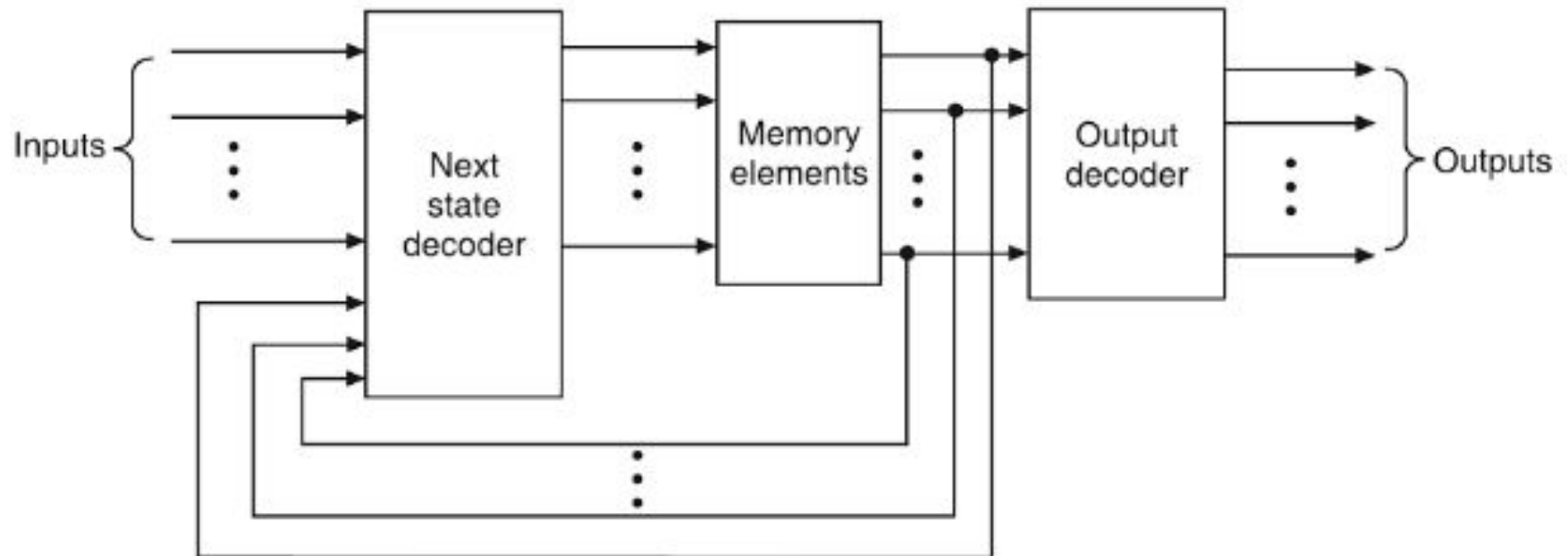


Fig: Moore circuit model

# Group Discussion and Report Back (Pen): Mealy and Moore Models

- Using the provided circuit models, identify at least 3 differences between the Mealy and Moore models.

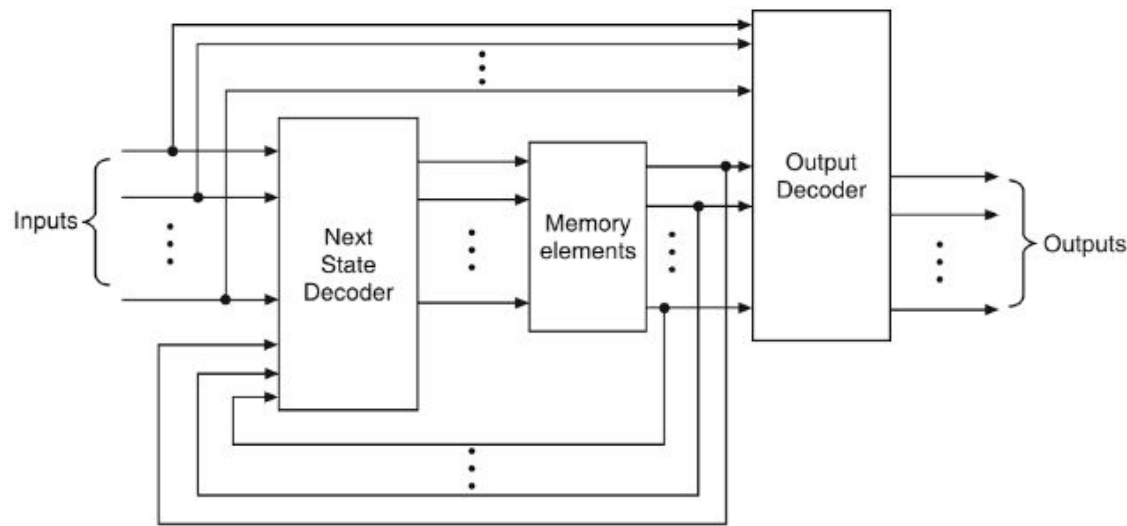


Fig 1: Mealy circuit model

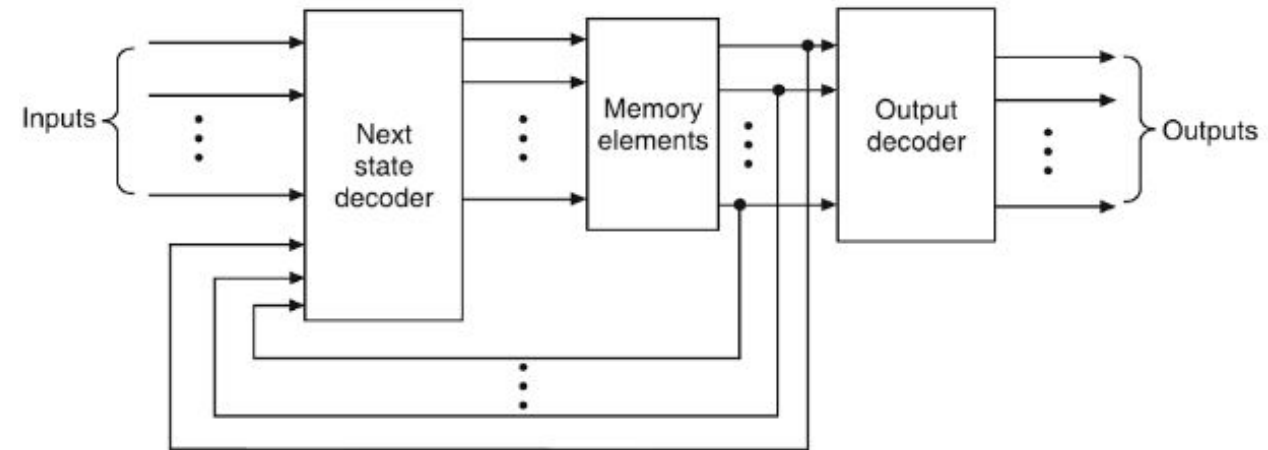


Fig 2: Moore circuit model

# Sequence Detector for Moore Model

- Sequence detector for 01 or 10.
- Output 1 when the sequence is seen
- Moore Model: Output is a function of only state

 


Fig: State diagram

reset	input	current state	next state	output
1	—	—	A	
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	D	0
0	0	C	E	0
0	1	C	C	0
0	0	D	E	1
0	1	D	C	1
0	0	E	B	1
0	1	E	D	1

Fig: State table

# Sequence Detector for Mealy Model

- Sequence detector for 01 or 10
- Output 1 when the sequence is seen
- Mealy Model: Output is a function of state and inputs

 


Fig: State diagram

reset	input	current state	next state	output
1	–	–	A	0
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	C	1
0	0	C	B	1
0	1	C	C	0

Fig: State table

# Homing Sequence

Homing sequence is  $X=101$ , since the final state can be uniquely determined by observing outputs.

Starting at A, we end-up in state C with outputs 100

Starting at B, we end-up in state A with outputs 100

Starting at C, we end-up in state B with outputs 101


Starting at D, we end-up in state C with outputs 011

Present State	Input X=0	Input X=1
A	C,1	D,0
B	D,0	B,1
C	B,0	C,1
D	C,0	A,0

If we observe outputs, at the end of 3<sup>rd</sup> input, we know the current state, even though the initial state was unknown
 
# Distinguishing Sequence

- A sequence  $X$  is a distinguishing sequence for machine  $M$  if the output sequence produced in response to  $X$  is distinct for each initial state.
- Distinguishing = separating for nondeterministic machines
- A distinguishing (input) sequence  $\alpha$  allows to determine the initial state of the machine under experiment
- After applying  $\alpha$  at any state  $s$  and observing an output response  $\beta$  the initial state  $s$  becomes known



$$out(s_i, \alpha) \cap out(s_j, \alpha) = \emptyset$$

Fig: Distinguishing sequence  $\alpha$



# Synchronizing Sequence

- A synchronizing sequence is a sequence of inputs that will force the machine to a specified final state independent of the initial state or output sequence.
- A synchronizing sequence  $\alpha$  takes the machine under experiment to a given state after applying  $\alpha$
- After applying  $\alpha$  at any state the final state is  $s'$

 


Fig: Synchronizing sequence  $\alpha$

# Summary of this Lesson

- Answer questions related to Project 1: Finite State Machines in Verilog
  - Due in Lesson 10

# Post-work for Lesson 5

## Homework

- After the Live Lecture, you will complete and submit a homework assignment. Go to the online classroom to view and submit the assignment.

# To Prepare for the Next Lesson

- Read the Required Readings for Lesson 4.
- Complete the Pre-work for Lesson 4.
- Continue working on the Project.

**Go to the online classroom for details.**