

ECE 697CE Foundations of Computer Engineering

Lesson 2

Boolean Switching Functions (Continued)

© 2017 UMass Amherst Global. All rights reserved.



Rationale

- Threshold logic forms the basis of neural computing
- Minimizing switching functions helps overcome limitations of switching algebra
- Minimization also creates more effective expressions



Objectives

- Understand Electronic Gate Networks
- Differentiate between functions of threshold elements
- Apply principles of minimization to simplify switching functions
- Compare the properties of unate, monotonic, and symmetric functions



Poll: Prior Knowledge

The following is an example of what principle of Boolean Switching Functions?

$$[f(x_1, x_2 x_n, 0, 1, +,.)]' = f(x_1', x_2' x_n', 1, 0, .., +)$$

- 1. Combinational Switching Logic
- 2. De Morgan's Theorem
- 3. Law of Complementation
- 4. Consensus Theorem



Prior Knowledge

- Let's review from Lesson 1: Boolean Switching Functions
 - Number representation
 - Switching logic & algebra
 - Simplification of expressions
 - De Morgan's Theorems



Orchestrated Discussion (Hand Raise): Critical Thinking Exercise

Discuss two questions regarding Lesson 1.



Electronic Gate Networks

- <u>Electronic gates</u>: generally receive voltages as inputs and produce output voltages
- Precise values of voltages not significant: restricted to value ranges – high (value 1) and low (value 0)
- Electronic gates constructed with two-state switching devices: each capable of permitting the flow of current or blocking it
- To implement arbitrary switching functions: gates must be able to implement a functionally complete set of operations

Fig: Gate symbols



Threshold Logic

- Simplest kind of computing units in Artificial neural networks
- Operate by comparing total input with a threshold
- Generalization of the common logic gates in conventional computing



The Threshold Element

n two valued inputs :

$$x_1, x_2, ... x_n$$

- Single two valued output: y
 - Internal parameters
 - Threshold: T
 - Weights: $w_1, w_2, ... w_n$



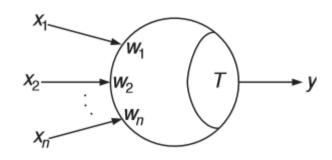



Fig: Symbol for a threshold element



Input-Output Relation of a Threshold Element

Input Output relation of a threshold element
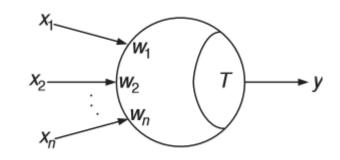
$$y = 1 if and only if \sum_{i=1}^{n} w_i x_i \ge T$$



$$y = 0$$
 if and only if $\sum_{i=1}^{n} w_i x_i < T$

• $\sum_{i=1}^{n} w_i x_i$: Weighted sum of the element



Example: A Threshold Element

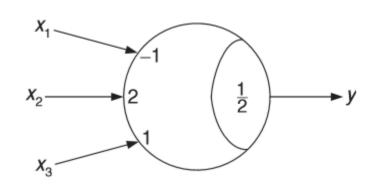


Fig: A threshold element

Input variables		les	Weighted sum	Output
x_1	x_2	x_3	$-x_1 + 2x_2 + x_3$	у
0	0	0	0	0
0	0	1	1	1
0	1	0	2	1
0	1	1	3	1
1	0	0	-1	0
1	0	1	0	0
1	1	0	1	1
1	1	1	2	1

Table: Input Output relation of the gate

Switching function realized

$$f(x_1, x_2, x_3) = \sum (1, 2, 3, 6, 7) \Rightarrow simplify \Rightarrow x_1'x_3 + x_2$$



Majority Gates

- Special type of threshold element
- Property of a 3 input majority gate:

Produces a 1 if majority of inputs are 1
$$M(x_1, x_2, x_3) = x_1x_2 + x_2x_3 + x_3x_1$$

Implementation as a threshold element

$$w_1 = w_2 = w_3 = 1$$
 and $T = 2$

- To implement an AND gate: Tie one input to 0
- To implement an OR gate: Tie one input to 1



Minority Gates

Property of a 3 input minority gate:

Produces a 1 if majority of inputs are 0
$$m(x_1, x_2, x_3) = x_1'x_2' + x_2'x_3' + x_3'x_1'$$

- Complement of Majority function
- To implement a NAND gate: Tie one input to 0
- To implement a NOR gate: Tie one input to 1



Minimization of Switching Function

- Aim: Simplify switching function $f(x_1, x_2, ... x_n)$ to find an expression $g(x_1, x_2, ... x_n)$ which is equal to f and minimizes some cost criteria
- Criteria to determine minimal cost:
 - Minimum number of appearances of literals
 - Minimum number of literals in SOP or POS expression
 - Minimum number of terms in SOP expression (Ensure there is no other expression with same number of terms and fewer literals)



Irredundant Expression

 Irredundant expression: A SOP expression from which no term can be deleted without altering its logic

•
$$f(x,y,z) = x'yz' + x'y'z' + xy'z' + x'yz + xyz + xy'z$$
 -> Redundant
= $x'z' + y'z' + yz + xz$ -> Irredundant

- An irredundant expression is not necessarily minimal
- Minimal expression not always unique



Whiteboard: Irredundant Expression

• a + a'b is irredundant but not minimal. a+a'b = a+b. a+b is minimal.

• ab' + ac' + a'c + a'bc' = b'c + a'b + ac' realize the same function but different expressions.



Karnaugh Map: The Map Method

 Algebraic method to combine terms using the rule

$$Aa + Aa'$$

- Modified form of truth table
- Arrangement of combinations is conver
- n-variable map consists of 2^n cells
- Cells represent all possible combinations of variables

\wx	,			
yz	00	01	11	10
00	0	4	12	8
01	1	5	13	9
11	3	7	15	11
10	2	6	14	10

Fig: Location of minterms in 4 variable map


yz wx	00	01	11	10
00		1	1	1)
01		1	1	
11			1	
10			1	

Map for $f(w, x, y, z) = \sum (4, 5, 8, 12, 13, 14, 15)$



Minimization of Boolean Functions

- Box: Collection of 2^m cells, each adjacent to m cells of the collection.
- Box is said to <u>cover</u> these cells
- Expressed as a product of n-m literals for a function containing n variables
- Eliminate m literals that are not in the product
- Make as many boxes as possible and as large as possible.
- Boxes can only have dimensions of 1, 2, or 4.
- Each box represents 1 term.
- Doubling the size of a box reduces 1 literal from that term.

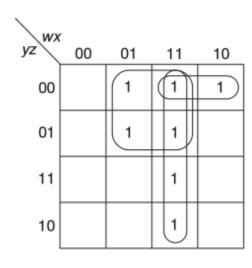


Map for $f(w, x, y, z) = \sum (4, 5, 8, 12, 13, 14, 15)$



Minimization of Boolean Functions

• Example : f = yz' + xy

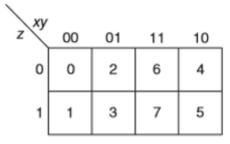

z xy 00 01 11 10 0 1 1 1 1 10

Fig: Location of minterms in a three variable map

Fig: Map for function f(x, y, z) = yz' + xy

Algebraic manipulations:

$$f = x'yz' + xyz' + xyz$$

$$= x'yz' + xyz' + xyz' + xyz$$

$$= yz'(x' + x) + xy(z' + z)$$

$$= yz' + xy$$



Rules for Minimizations of Boolean Functions

- Cover with boxes those 1-cells that cannot be combined with any other 1-cell.
- Continue to those which have only a single adjacent 1-cell and thus can form boxes of only two 1-cells
- Combine those 1-cells that yield boxes of four but not part of any box of eight cells, and so on
- Minimal expression:
 - A collection of boxes that are as large and as few in number as possible
 - Every 1-cell in the map of the function is covered by at least one box.



Whiteboard: Minimization Example

• Two irredundant expressions $f(w, x, y, z) = \sum (0, 4, 5, 7, 8, 9, 13, 15)$

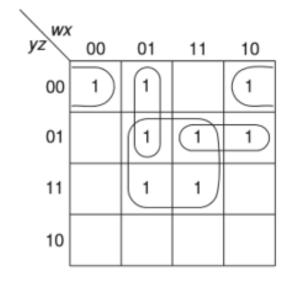


Fig: f = x'y'z' + w'xy' + wy'z + xz is an irredundant expression

yzwx	(
y2 \	00	01	11	10
00	1	1		1
01		1	1	1
11		1	1	
10				

Fig: f = w'y'z' + wx'y' + xzis the unique minimal expression



Summary of this Lesson

Learned about simplification of logic functions



To Prepare for the Next Lesson

- Read the Required Readings for Lesson 3.
- Complete the Pre-work for Lesson 3.

Go to the online classroom for details.